

# Important test results and final testing outcomes

## 1. Basic Circuit

- 1.1. Initially, we started by directly giving a voltage, controlled by a potentiometer, to the non-inverting input of the op-amp, with the op-amp output connected to the gate of an NMOS transistor (using a single circuit). For the circuit diagram, refer to the design documentation.
- 1.2. We noted that the current was varying over a small voltage range, due to the quadratic characteristics of MOSFETs. This made it difficult to have fine control over the current value.
- 1.3. Because of this, we moved towards BJT. Here, we observed that the maximum value of current reached was  $\sim 2.5\text{A}$ . So, we decided to have two circuits in parallel.

## 2. Integrating with microcontroller

- 2.1. Then, we gave the non-inverting voltage through a DAC controlled by an STM microcontroller.
- 2.2. This required some fine-tuning of the parameters in the microcontroller code.

## 3. CC-CV switching

- 3.1. For CC-CV switching, we first tried implementing a switch using an MOS transistor. This malfunctioned in our fabricated PCB.
- 3.2. Then, we used current control to maintain constant compliance voltage across the load in CV mode.

## 4. Implementing UART

- 4.1. We also included control of current using UART.
- 4.2. This can accurately read and write the current values.